
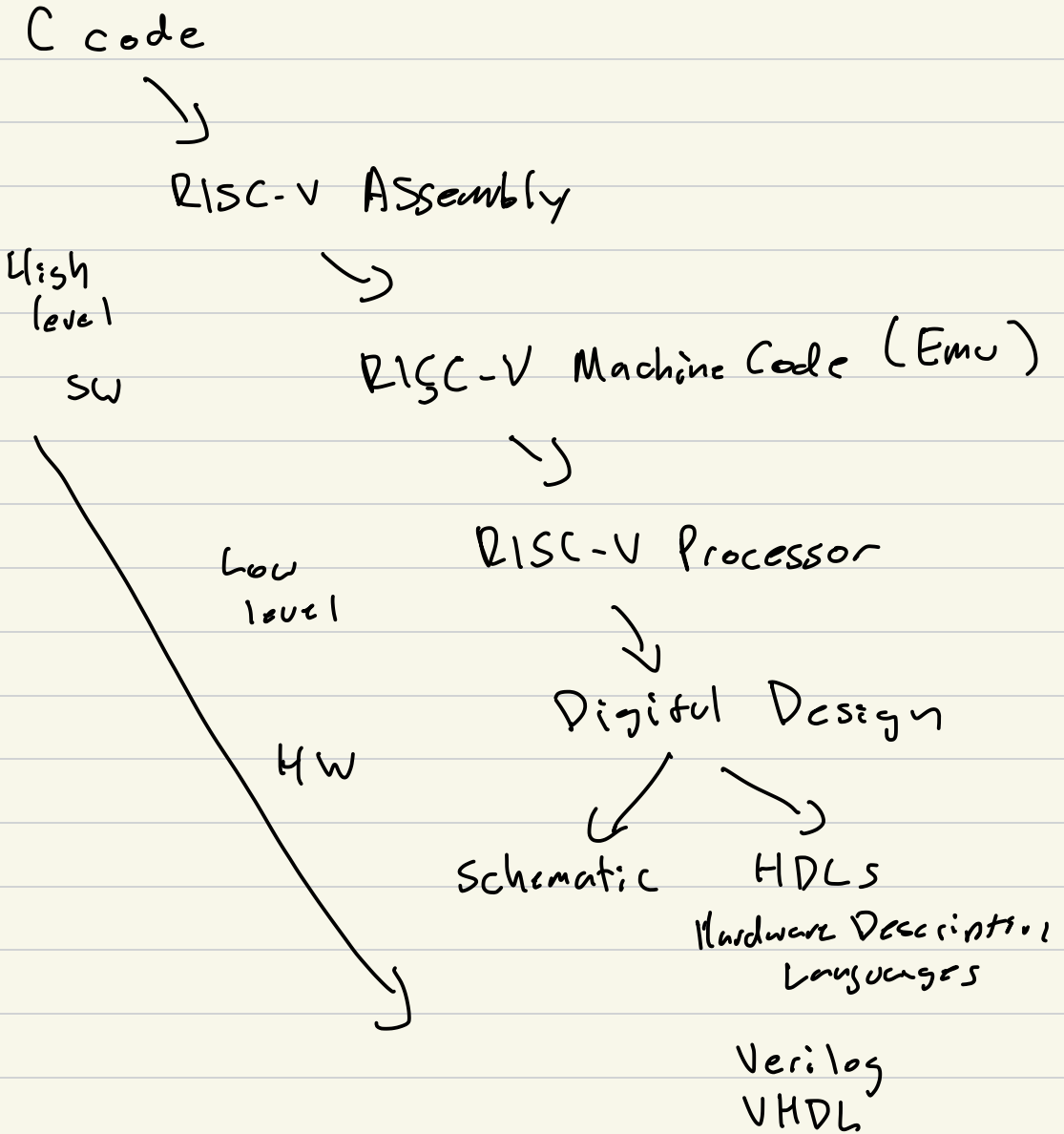



# CS 631-01 Digital Design

## Combinational Logic

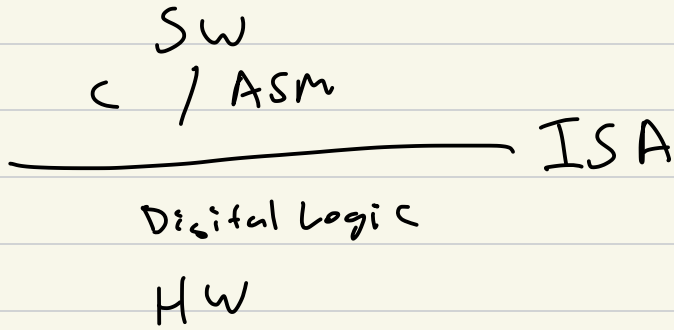






Analog  $\rightarrow$  Digital

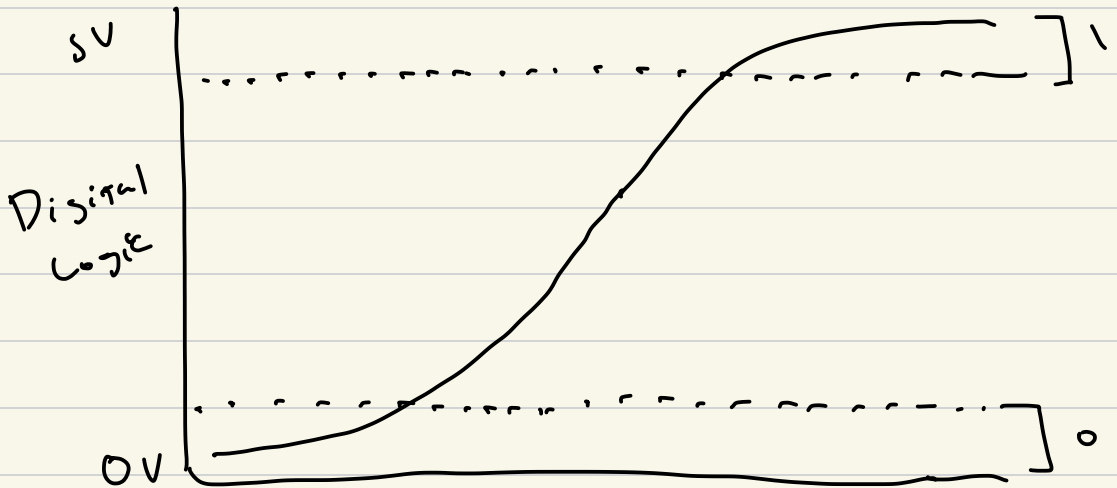

Wires

devices  $\rightarrow$  gates

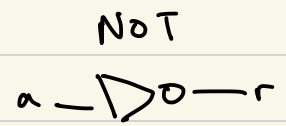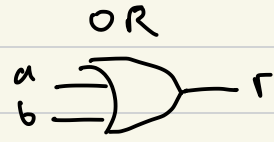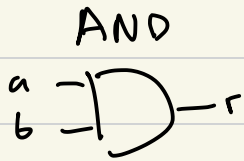

C

$$r = a \& b$$

$$r = a | b$$

$$r = \sim a$$

Boolean Algebra

$$r = a \cdot b$$

$$r = a + b$$

$$r = \bar{a}$$

Logic

$$r = a \wedge b$$


$$r = a \vee b$$

$$r = \neg a$$

a	b	r
0	0	0
0	1	0
1	0	0
1	1	1


a	b	r
0	0	0
0	1	1
1	0	1
1	1	1

a	r
0	1
1	0

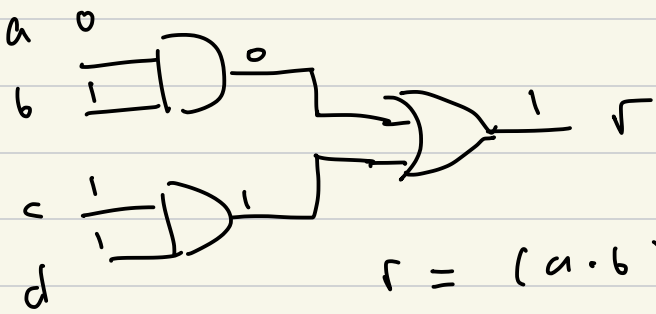

$$r = (a \cdot b) + (c \cdot d)$$

# Goal

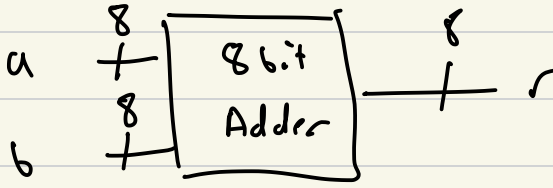


## Sum-of-products

Sum of two 1-bit numbers

$$\text{XOR Sum} = a \oplus b$$

	a	b	Sum
	0	0	0
①	0	1	1
②	1	0	1
	1	1	0
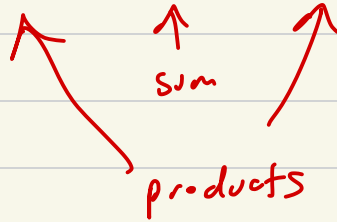
$$\text{Sum} = (\bar{a} \cdot b) + (a \cdot \bar{b})$$




$$a = 0 \quad b = 1$$

$$\text{Sum} = (\bar{0} \cdot 1) + (0 \cdot \bar{1})$$

$$= (1 \cdot 1) + (0 \cdot 0)$$

$$= 1 + 0$$


$$= 1$$

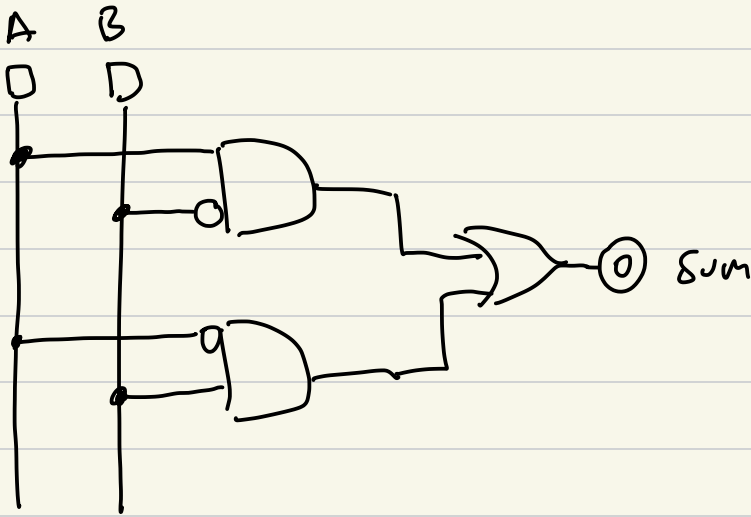

## Sum-of-products

- i) Define your function
- 2) Build a truth table
- 3) Identify rows with output = 1
- 4) Construct product terms for each row
  - a) don't invert if input is 1
  - b) invert if input is 0
- 5) Sum (+) all product terms

# 1 bit full adder

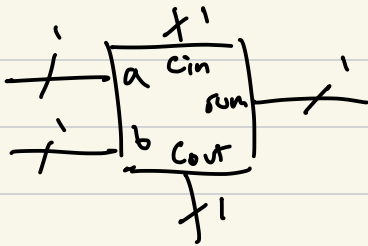

	a	b	cin	sum	cout
	0	0	0	0	0
①	0	0	1	1	0
②	0	1	0	1	0
	0	1	1	0	1
③	1	0	0	1	0
	1	0	1	0	1
	1	1	0	0	1
	1	1	1	1	1

$$\text{Sum} = (\bar{a} \cdot \bar{b} \cdot c_{in}) + (\bar{a} \cdot b \cdot \bar{c}_{in}) + (a \cdot \bar{b} \cdot \bar{c}_{in}) + (a \cdot b \cdot c_{in})$$

a b c:n

