

CS 621-01 Digital Design

Sequential Logic

Lab 06 Testing

Goal N-bit Register

SR Latch



Clock



D Latch



D Latch with CLR



Multiplexors



D flip-flop






D flip-flop CLR EN → 1 bit Register



N-bit Register



Static
RAM

SR Latch Set Reset

   


R	S	Q	Q̄
0	0	0	1
0	1	1	0
0	0	1	0
1	0	0	1
0	0	0	1
1	1	XX	


SR Latch

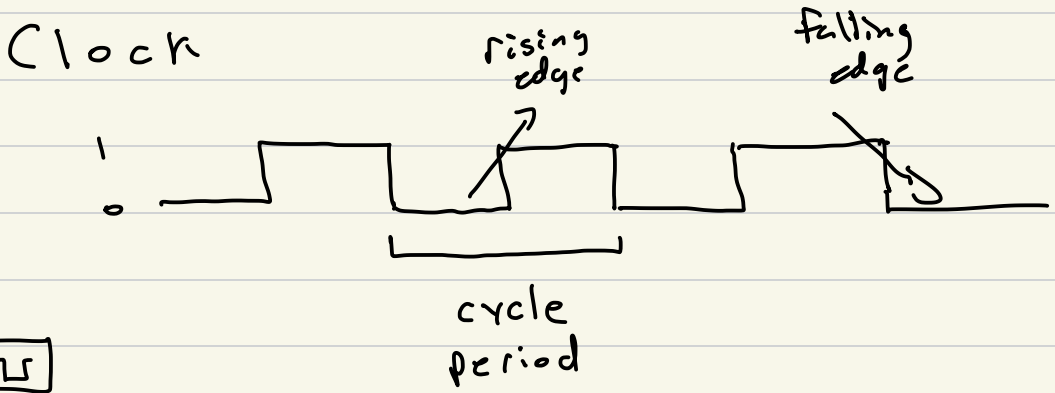 

D Latch


 



D Latch with CLR

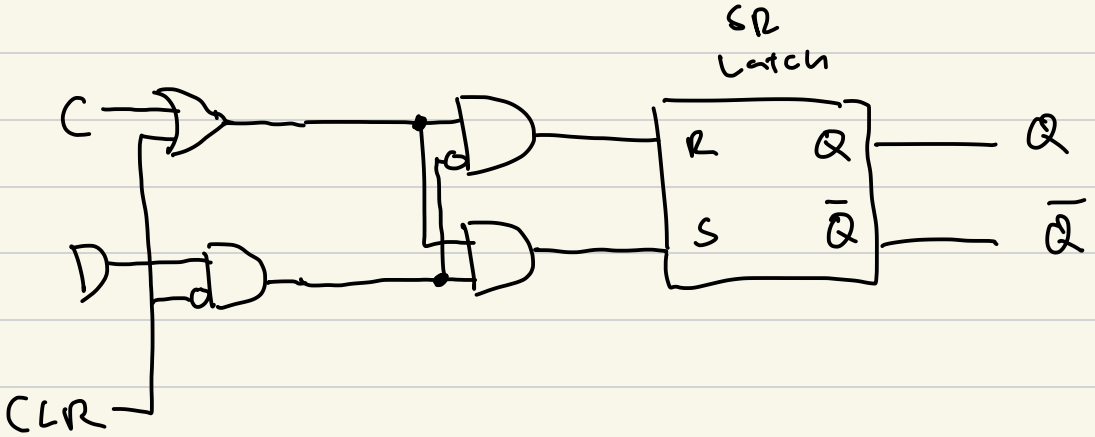



Multiplexor

a	b	s	r
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 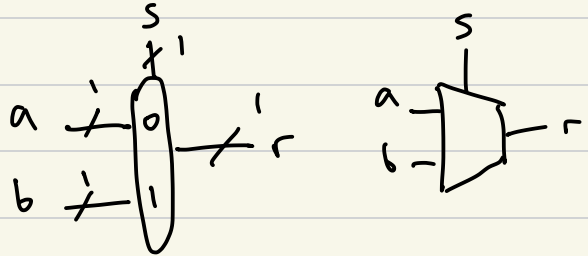

 

D flip-flop rising edge

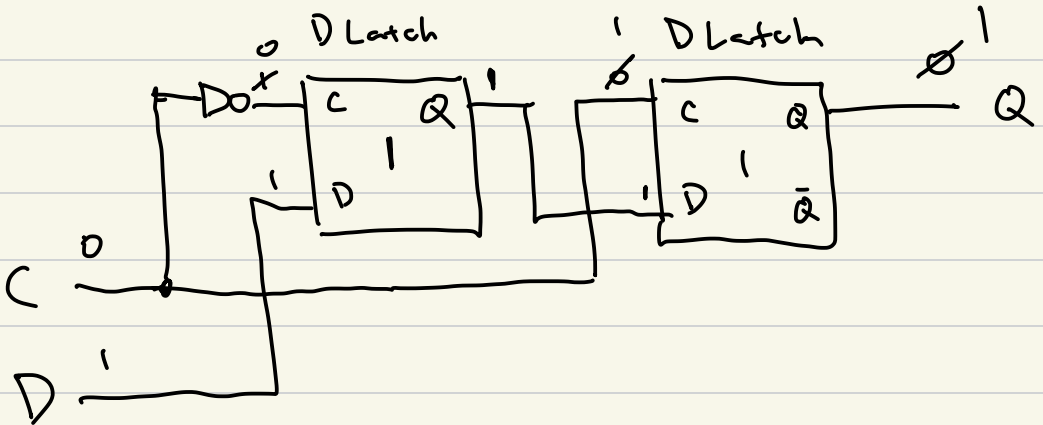 

D flip-flop with \overline{CR} and \overline{EN}