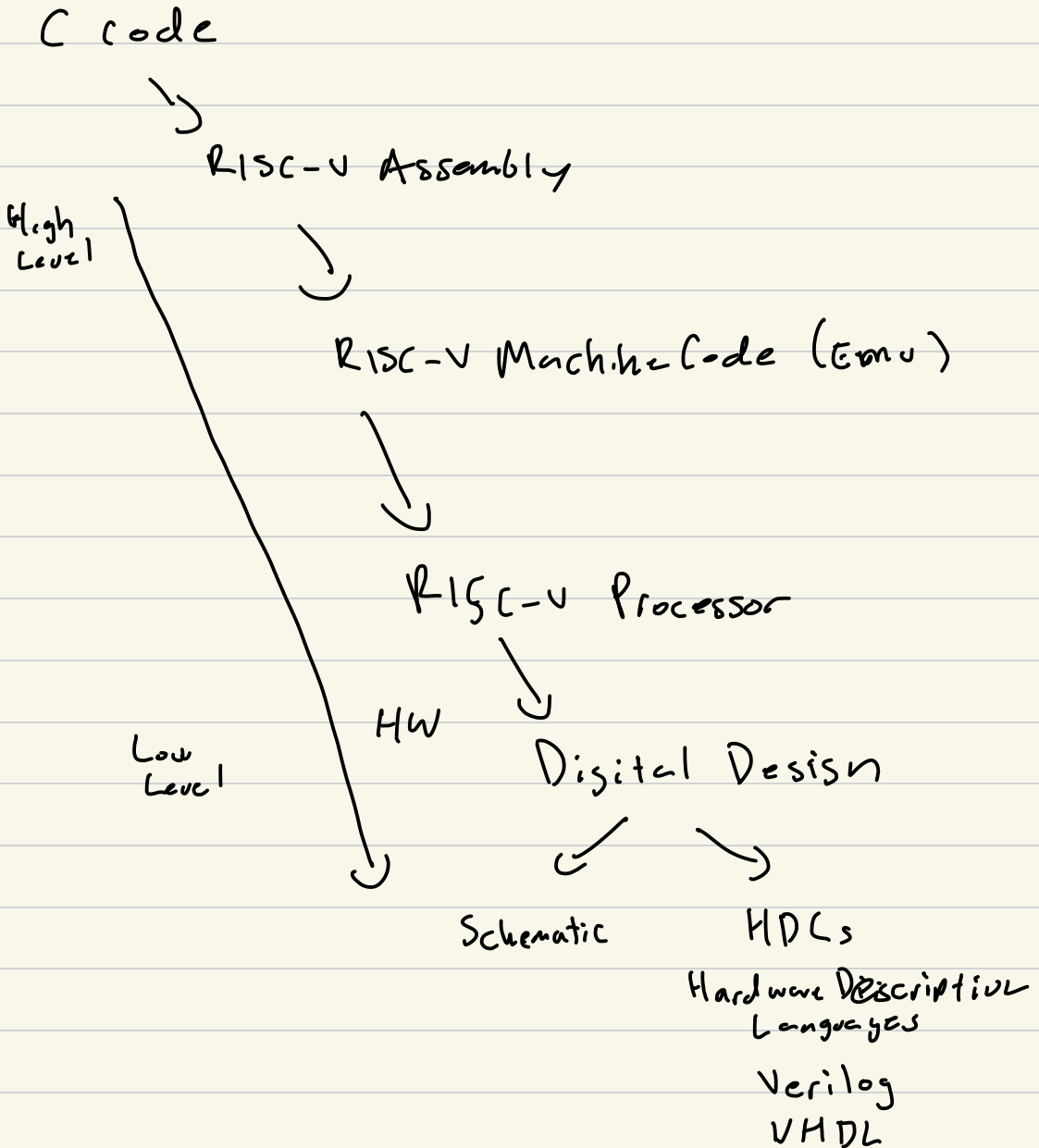


CS 631-02 Digital Design

Combinational Logic




SW
C / ASM

ISA

HW

Digital Logic


Analog

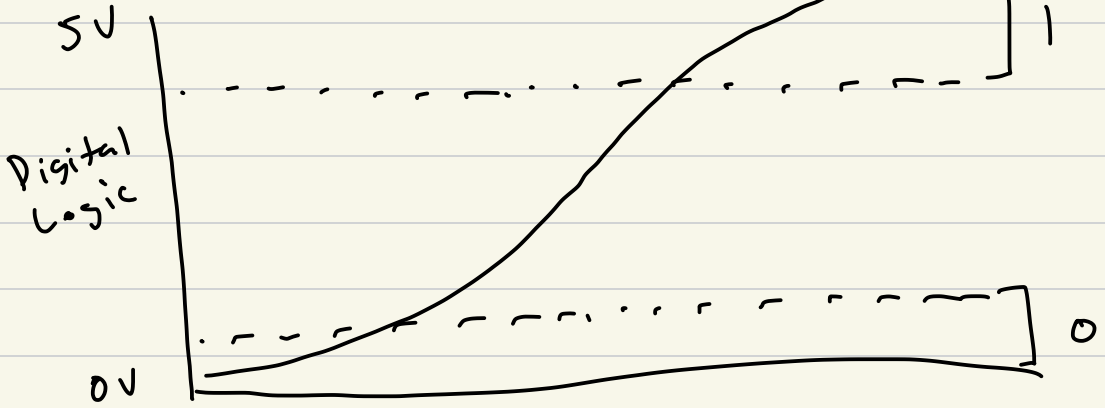


Wires

Device \rightarrow gates


AND

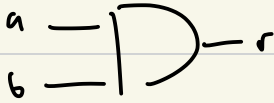

OR

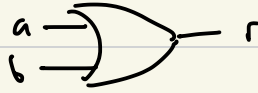

NOT

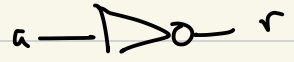

C

$$r = a \& b$$

$$r = a | b$$

$$r = \neg a$$

Boolean Algebra

$$r = a \cdot b$$

$$r = a + b$$

$$r = \bar{a}$$

Logic

$$r = a \wedge b$$

$$r = a \vee b$$


$$r = \neg a$$

a	b	r
0	0	0
0	1	0
1	0	0
1	1	1

a	b	r
0	0	0
0	1	1
1	0	1
1	1	1

a	r
0	1
1	0


inclusive

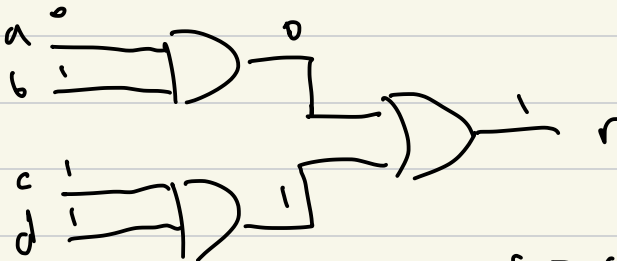

Combinational Logic

$$r = (a \cdot b) + (c \cdot d)$$

Goal

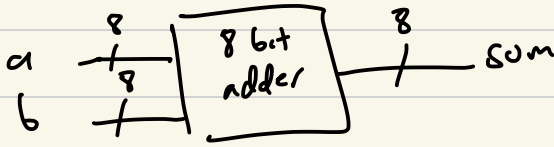


Sum-of-products

Sum two 1-bit numbers

$$\text{XOR sum} = a \oplus b$$


	a	b	sum
	0	0	0
①	0	1	1
②	1	0	1
	1	1	0
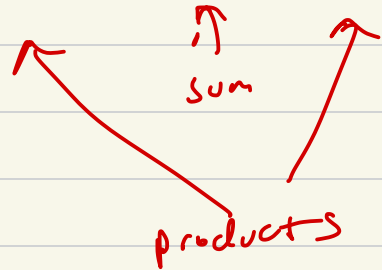
$$\text{sum} = (\bar{a} \cdot b) + (a \cdot \bar{b})$$



$$a = 0 \quad b = 1$$


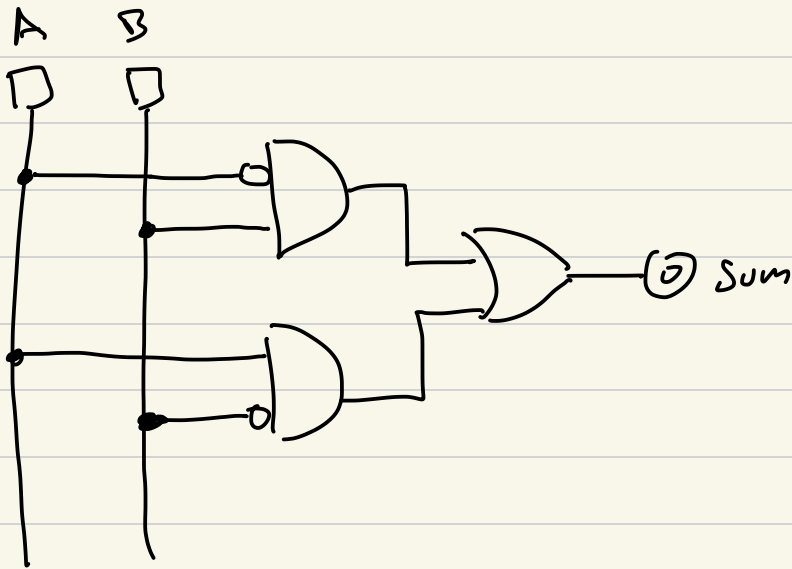
$$\begin{aligned} \text{sum} &= (\bar{0} \cdot 1) + (0 \cdot \bar{1}) \\ &= (1 \cdot 1) + (0 \cdot 0) \\ &= \overbrace{1}^1 + 0 \\ &= 11 \end{aligned}$$



Sum-of-products

- 1) Define your function
- 2) Build a truth table
- 3) Identify rows with output = 1
- 4) Construct product terms for each row (3)
 - a) don't invert if input is 1
 - b) invert if input is 0
- 5) Sum (+) all product terms

1 bit Full adder

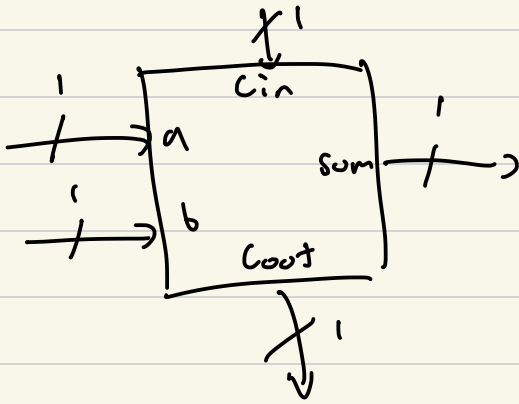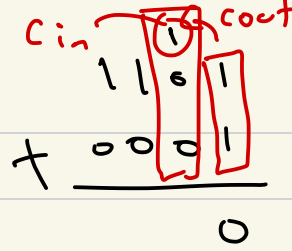

	a	b	cin	sum	cout
	0	0	0	0	0
(1)	0	0	1	1	0
(2)	0	1	0	1	0
	0	1	1	0	1
(3)	1	0	0	1	0
	1	0	1	0	1
	1	1	0	0	1
(4)	1	1	1	1	1

$$\text{sum} = (\bar{a} \cdot \bar{b} \cdot c_{in}) + (\bar{a} \cdot b \cdot \bar{c}_{in}) + (a \cdot \bar{b} \cdot \bar{c}_{in}) + (a \cdot b \cdot c_{in})$$

